

## Electrical Engineering Workshop (ইলেকট্রিক্যাল ইঞ্জিনিয়ারিং) 3 hours/day

### Week 1: From Electrons to Circuits (ইলেকট্রন থেকে সার্কিট)

#### Lesson 1.3: Fundamentals of Electricity: Diodes, How to Use a Breadboard, and Designing Simple Circuits

(ইলেকট্রনিক্সের মূলসূত্র)

<ul style="list-style-type: none"> <li>• RECAP: R, L, C in series and parallel; R, L, C behavior with AC and DC               <ul style="list-style-type: none"> <li>○ Any questions?? Better ask now because I'll soon be testing your understanding!</li> </ul> </li> </ul>	<ul style="list-style-type: none"> <li>• 10 m</li> </ul>
<ul style="list-style-type: none"> <li>• MINI-QUIZ! Erase everything on the board and give them a mini quiz to test understanding from first two classes.</li> </ul>	<ul style="list-style-type: none"> <li>• 10 m</li> </ul>
<ul style="list-style-type: none"> <li>• RECALL: Remember we talked about AC signals?               <ul style="list-style-type: none"> <li>○ DRAW: Graph of AC signal with voltage going positive and negative.</li> <li>○ DRAW: Circuit with AC voltage connected to resistor.</li> <li>○ POSE QUESTION: What does the voltage look like across the resistor? Same as the graph I just drew right? What if I don't want any negative voltage across my resistor? What if I want just positive? (Draw desired output) I need another component right? Can I make that happen with R, L, and C's?</li> <li>○ GUIDE THROUGH: what happens if we put an R, L, or C between the VAC and the R? Do any of these work? DRAW graphs of voltage across R for each inserted R, L, or C.</li> <li>○ WORKSHEET: Explain why we might want to only allow current to flow one way. Also students draw graphs as we go through the examples on the board.</li> </ul> </li> </ul>	<ul style="list-style-type: none"> <li>• 10 m</li> </ul>
<ul style="list-style-type: none"> <li>• NEW CONCEPT: None of those components worked, so we need a new component! This component is called a diode. A diode only allows current to flow one way, and it blocks negative voltage. It only allows current in the direction of the arrow.               <ul style="list-style-type: none"> <li>○ VOCABULARY: The back of the arrow is called the anode. The front of the arrow is called the cathode.</li> <li>○ DRAW: Trace over graph of input to show what parts the diode will allow to pass and how it blocks negative current.</li> <li>○ DRAW: Draw over schematic to show direction of current allowed and draw what happens (open circuit) when the voltage turns negative</li> <li>○ ASK: Can someone come up and draw the voltage across the resistor with the diode in between?</li> <li>○ CHALLENGE ASK: Can someone come up and draw the voltage across the resistor with the diode in between but in the opposite direction? GUIDE whoever comes up in drawing the graph.</li> <li>○ WORKSHEET: Drawing graphs of voltage output in diode circuits.</li> </ul> </li> </ul>	<ul style="list-style-type: none"> <li>• 10 m</li> </ul>
<ul style="list-style-type: none"> <li>• RECALL: Remember how we talked about an LED: That stands for Light Emitting Diode. And that's also why the schematic symbol looks almost just like the diode schematic symbol!               <ul style="list-style-type: none"> <li>○ ASK: Someone remind us, what does an LED do?</li> <li>○ POSE QUESTION: If we are able to emit light by flowing a current through an LED, do you think that we can create the reverse type of component? Can we have a component that, when we shine light on it, it causes current to flow? What are your thoughts?</li> </ul> </li> </ul>	<ul style="list-style-type: none"> <li>• 10 m</li> </ul>
<ul style="list-style-type: none"> <li>• NEW CONCEPT: So yes, that component does exist and it's called a photodiode!               <ul style="list-style-type: none"> <li>○ DRAW: Diagram of P-N junction and show that when light hits, the photon's energy separates the electrons and holes, causing a current to flow. We will use a photodiode to make your heartbeat monitor!</li> <li>○ WORKSHEET: Draw and explain how a photodiode works.</li> </ul> </li> </ul>	
<ul style="list-style-type: none"> <li>• NEW CONCEPT: Now, there's one last type of diode I want to teach you about, and it's called a Zener diode.               <ul style="list-style-type: none"> <li>○ DRAW: In a circuit like this: Draw V, R, Z.</li> <li>○ EXPLAIN: A Zener diode always ensures that the voltage across its pins is a certain voltage. If it's a 4.7V Zener diode, then the voltage across the Zener diode must be 4.7V, and it will be able to take in very large amounts of currents to ensure this.</li> <li>○ ASK: Someone come up and use Ohm's Law to calculate the current that must be flowing through R and Z.</li> </ul> </li> </ul>	<ul style="list-style-type: none"> <li>• 10 m</li> </ul>

<ul style="list-style-type: none"> <li>○ WORKSHEET: Explain what a Zener diode does in your own words.</li> <li>● NEW CONCEPT: Breadboards! Explain importance of breadboards. <ul style="list-style-type: none"> <li>○ DRAW: Connections in breadboards.</li> <li>○ PASS AROUND: A breadboard with the backing open to show evidence of connections</li> <li>○ GUIDE STUDENTS THROUGH: Converting simple circuits to layout on breadboard. 3 examples. Method: Circle nodes, check off as you place each component on the breadboard.</li> <li>○ GUIDE STUDENTS THROUGH: Example with op-amp on breadboard – hooking up 8 pins to things.</li> <li>○ WORKSHEET: 2 conversions of circuits to breadboard layouts</li> </ul> </li> <li>● USE WEB APP: Students independently go through 5-10 breadboard layout challenges from assigned circuits. (Have 15 prepared) Be there to answer questions as students complete exercises.</li> <li>● DESIGN TIME: Design a circuit that can power one LED. <ul style="list-style-type: none"> <li>○ CHALLENGE: Now design a circuit that can power 5 LED's at once from one battery.</li> <li>○ GROUP THINKING: A third of the class does the LED's in series circuits. A third of the class does the LED's in parallel circuits. A third of the class does the LED-resistor combos in parallel circuits.</li> <li>○ ORDER: Make a hypothesis about what you think will happen for the circuit that you build. Then build it. Then record your results/observations.</li> <li>○ DISCUSS: Reconvene and ask each group to report their results from their explorations. Why did certain circuits work and certain other circuits didn't work?</li> </ul> </li> <li>● EXIT: Yay that's it! Everyone's exit ticket is a piece of paper with their (1) rating of the class, (2) list of up to three things they liked a lot, and (3) list of up to three things they didn't like and what they would like instead.</li> </ul>	<ul style="list-style-type: none"> <li>● 20 m</li> <li>● 40 m</li> <li>● 30 m</li> <li>● 5 m</li> </ul>
--	---